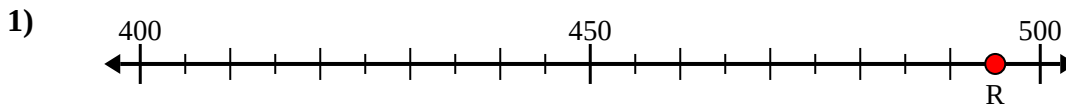





Trouvez la valeur de R

Réponses


1. _____




2. _____

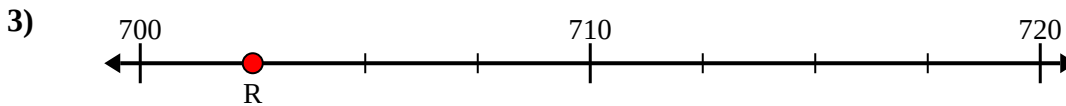


3. _____

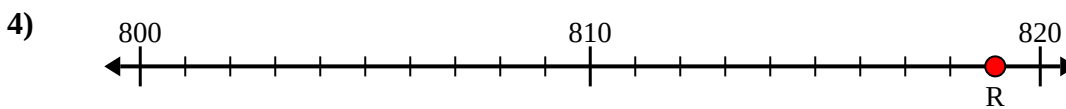


4. _____

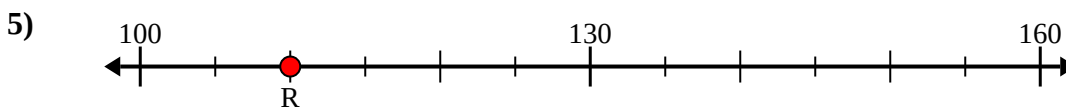


5. _____

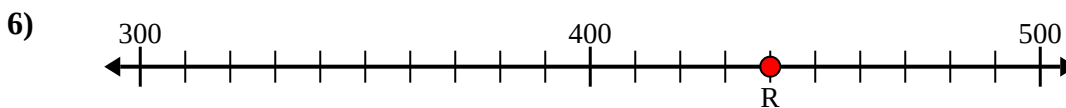


6. _____

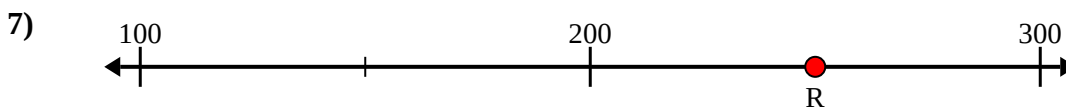


7. _____

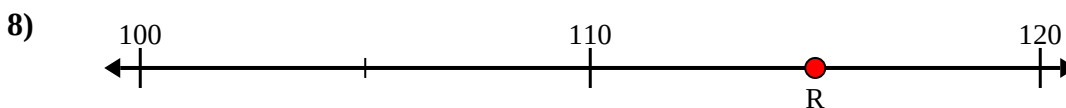

8. _____

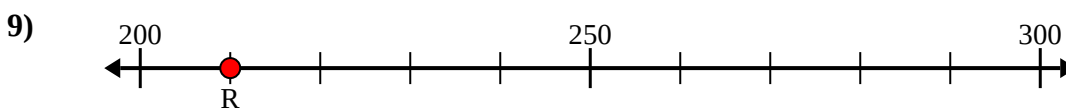










9. _____

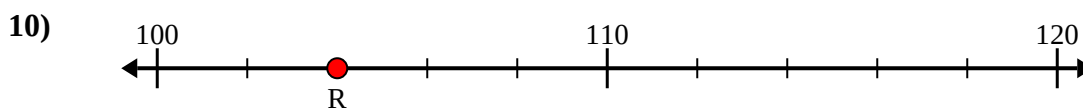

10. _____



Trouvez la valeur de R

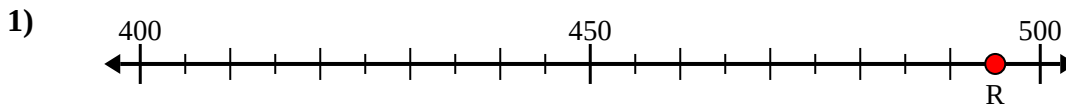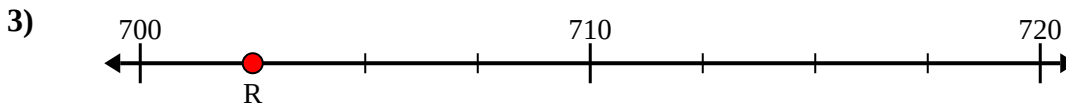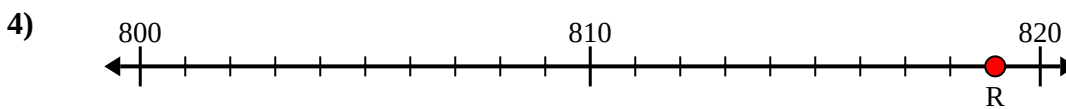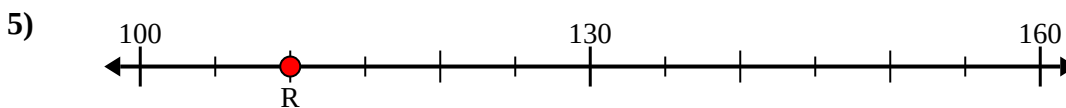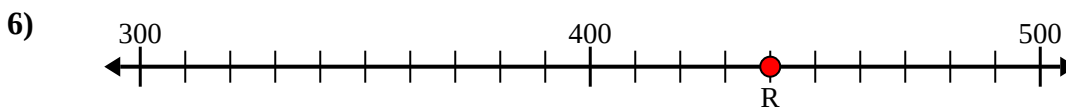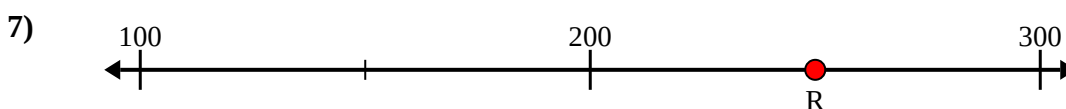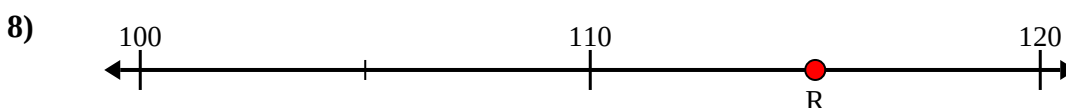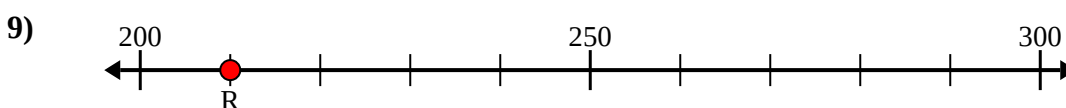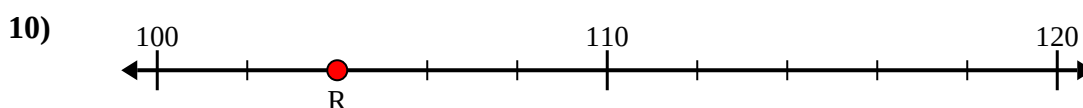Réponses1. **495**2. **490**3. **702,5**4. **819**5. **110**6. **440**7. **250**8. **115**9. **210**10. **104**