
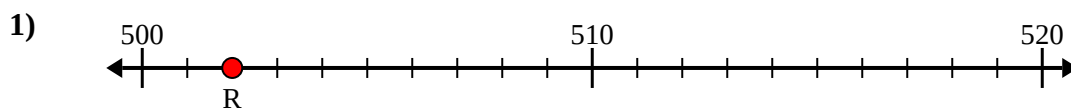


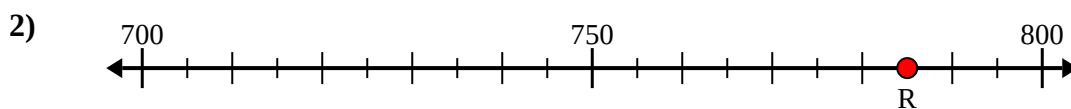


Trouvez la valeur de R

Réponses


1. _____




2. _____

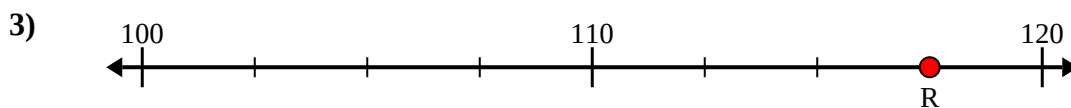


3. _____

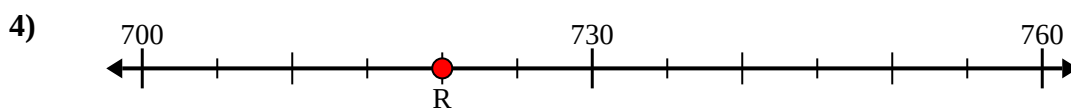


4. _____

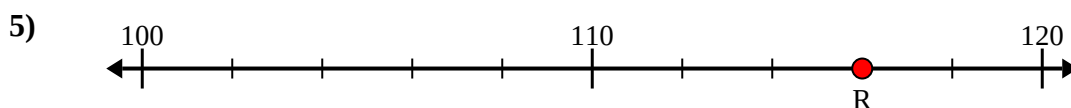


5. _____

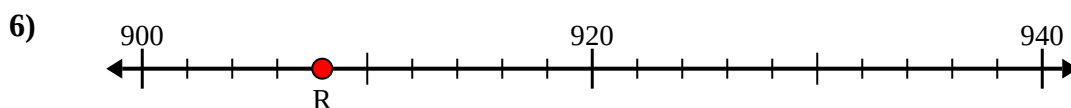


6. _____

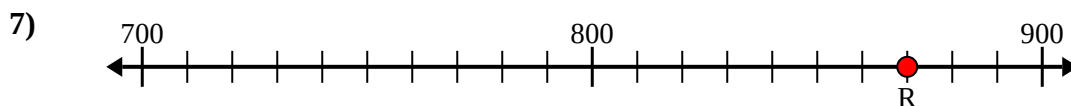


7. _____

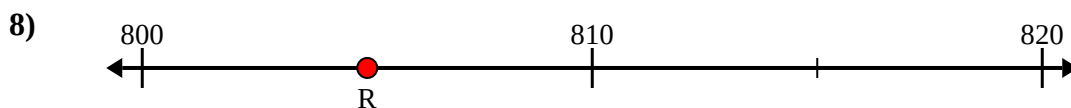

8. _____

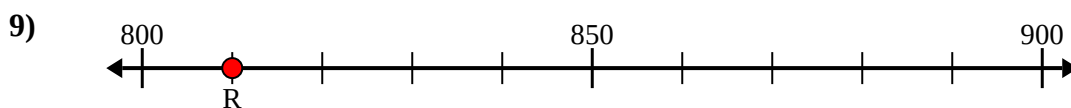











9. _____

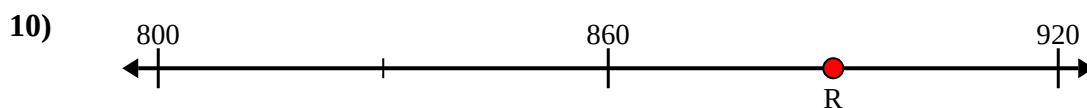

10. _____



Trouvez la valeur de R

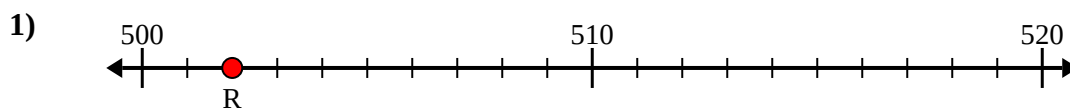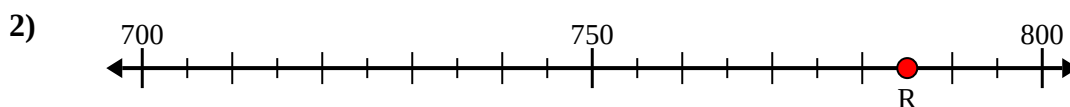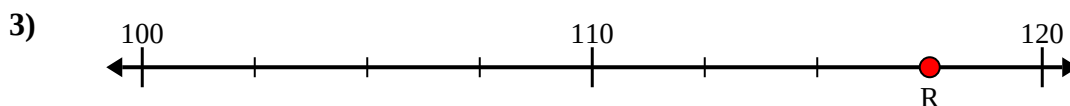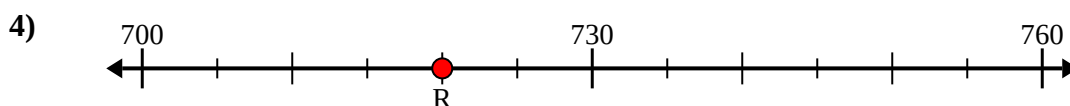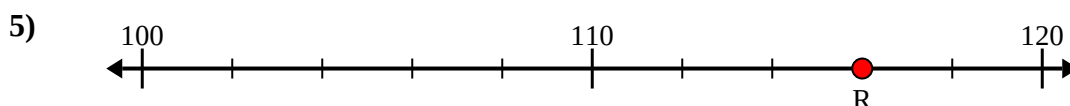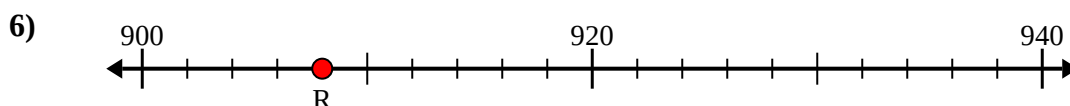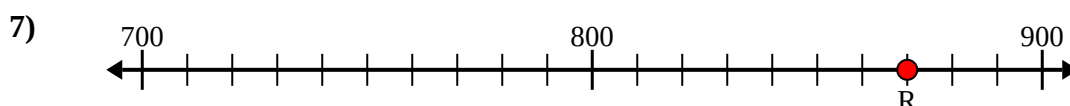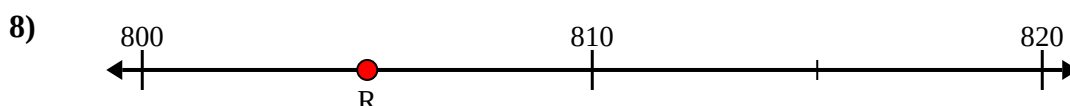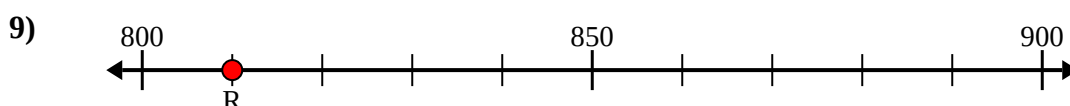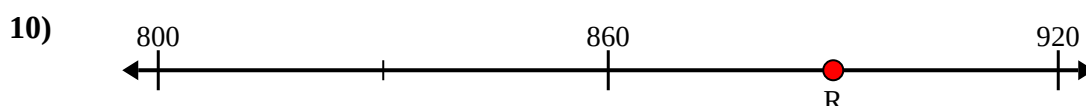Réponses1. **502**2. **785**3. **117,5**4. **720**5. **116**6. **908**7. **870**8. **805**9. **810**10. **890**